
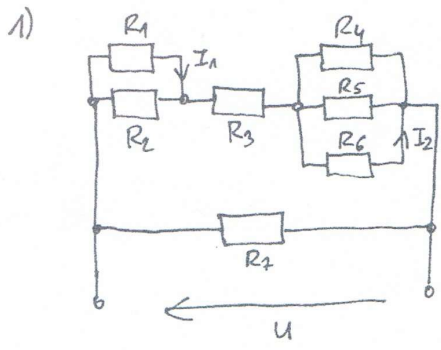


Prawo OHMA zadanie!

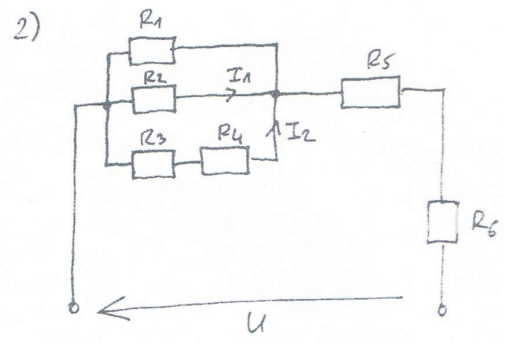


Dane: $R_1 = 3\Omega$
 $R_2 = 6\Omega$
 $R_3 = 2\Omega$
 $R_4 = R_5 = R_6 = 3\Omega$
 $R_7 = 5\Omega$
 $U = 2,5V$

Szukane: $I_1 = ?$
 $I_2 = ?$
 $R_2 = ?$




Dane: $R_1 = 10\Omega$
 $R_2 = 10\Omega$
 $R_3 = 2\Omega$
 $R_4 = 3\Omega$
 $R_5 = 2,5\Omega$
 $R_6 = 5\Omega$
 $U = 10V$

Szukane: $R_2 = ?$
 $I_1 = ?$
 $I_2 = ?$

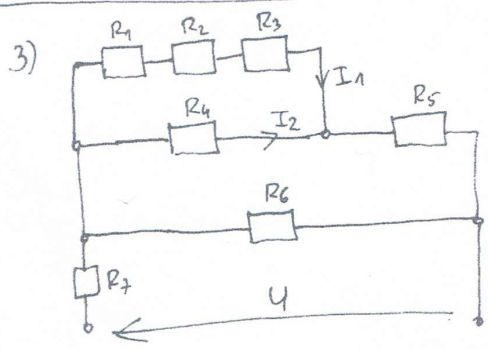


Dane: $R_1 = 2\Omega$
 $R_2 = 3\Omega$
 $R_3 = 5\Omega$
 $R_4 = 10\Omega$
 $R_5 = 5\Omega$
 $R_6 = 10\Omega$
 $R_7 = 2\Omega$
 $U = 7V$

Szukane: $R_2 = ?$
 $I_1 = ?$
 $I_2 = ?$

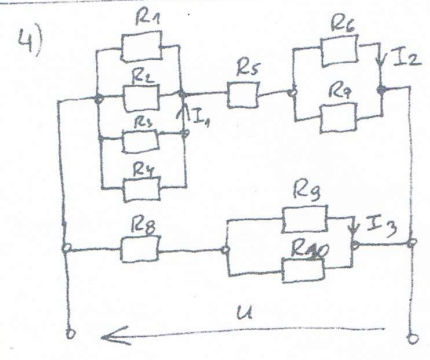


Dane: $R_1 = R_2 = R_3 = R_4 = 8\Omega$
 $R_5 = 3\Omega$
 $R_6 = 10\Omega$
 $R_7 = 10\Omega$
 $R_8 = 1\Omega$
 $R_9 = 18\Omega$
 $R_{10} = 18\Omega$
 $U = 10V$

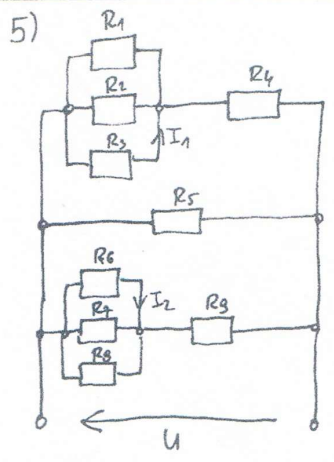Szukane: $R_2 = ?$
 $I_1 = ?$
 $I_2 = ?$
 $I_3 = ?$



Dane: $R_1 = 3\Omega$
 $R_2 = 6\Omega$
 $R_3 = 2\Omega$
 $R_4 = 4\Omega$
 $R_5 = 10\Omega$
 $R_6 = R_7 = 2\Omega$
 $R_8 = 10\Omega$
 $R_9 = 5\Omega$
 $U = 5V$

Szukane: $R_2 = ?$
 $I_1 = ?$
 $I_2 = ?$

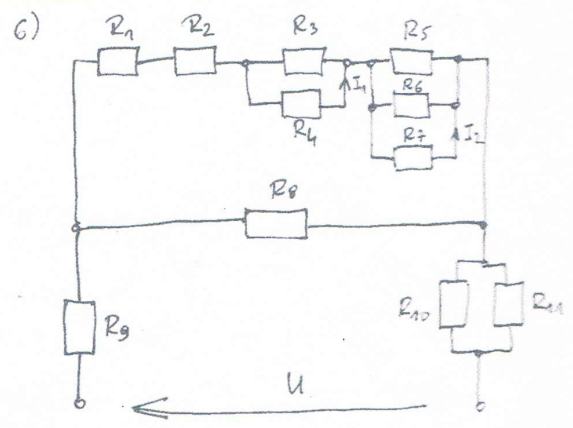

Dane: $R_1 = 1\Omega$
 $R_2 = 3\Omega$
 $R_3 = R_4 = 2\Omega$
 $R_5 = R_6 = R_7 = 3\Omega$
 $R_8 = 6\Omega$
 $R_9 = 1\Omega$
 $R_{10} = R_{11} = 8\Omega$
 $U = 8V$

Szukane: $R_2 = ?$
 $I_1 = ?$
 $I_2 = ?$